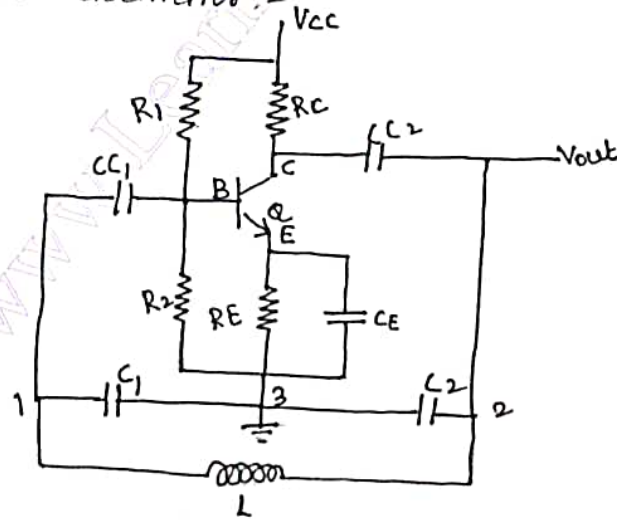


Colpitts Oscillator:-



Visit & Downloaded from : www.LearnEngineering.in
68

Visit & Downloaded from : www.LearnEngineering.in

→ In Colpitts Z_1 & Z_2 are the capacitors and Z_3 is an inductor. The resistors R_1 , R_2 and R_E provide the necessary dc bias to the transistor. The bypass capacitor is C_E . The coupling capacitors are C_1 & C_2 . The feedback network consisting of C_1 , C_2 & L determines the frequency of oscillator. Operation is similar to the Hartley Oscillator.

$$f = \frac{1}{2\pi\sqrt{L C_{eq}}} \quad \text{Where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Application:-

- 1) It is used for commercial signal generators for freq 1M to 800 MHz.
- 2) It is used as local oscillator in super heterodyne radio receiver.

Analysis:-

$$Z_1 = \frac{1}{j\omega C_1} = -\frac{j}{\omega C_1} \quad , \quad Z_2 = \frac{1}{j\omega C_2} = -\frac{j}{\omega C_2}$$

$$Z_3 = j\omega L$$

General form: $(Z_1 + Z_2 + Z_3)I_{net} + Z_1 Z_2 (H/L) + Z_1 Z_3 = 0$

Substituting Z_1 , Z_2 & Z_3 in above eqn

Visit & Downloaded from : www.LearnEngineering.in

$$hfe \left[\frac{-j}{\omega C_1} - \frac{j}{\omega C_2} + j\omega L \right] + \left(\frac{-j}{\omega C_1} \right) \left(\frac{-j}{\omega C_2} \right) (1+hfe) + \left(\frac{-j}{\omega C_1} \right) (j\omega L) = 0$$

$$hfe j \left[\omega L - \frac{1}{\omega C_1} - \frac{1}{\omega C_2} \right] - \frac{(1+hfe)}{\omega^2 C_1 C_2} + \frac{\omega L}{\omega C_1} = 0$$

$$jhfe \left[\omega L - \frac{1}{\omega C_1} - \frac{1}{\omega C_2} \right] + \left[\frac{L}{C_1} - \frac{(1+hfe)}{\omega^2 C_1 C_2} \right] = 0 \rightarrow (2)$$

Equating the imaginary part of eqn to zero

$$\omega L - \frac{1}{\omega C_1} - \frac{1}{\omega C_2} = 0 \rightarrow (3)$$

$$\omega L = \frac{1}{\omega C_1} + \frac{1}{\omega C_2}, \omega L = \frac{1}{\omega} \left[\frac{1}{C_1} + \frac{1}{C_2} \right]$$

$$\omega^2 = \frac{1}{L} \left[\frac{C_1 + C_2}{C_1 C_2} \right] \rightarrow (4)$$

$$\omega = \sqrt{\frac{C_1 + C_2}{L C_1 C_2}} \rightarrow (5)$$

$$f = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{L C_1 C_2}}$$

$$f = \frac{1}{2\pi \sqrt{L C_{eq}}} \rightarrow (6)$$

$$\text{where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2} \rightarrow (7)$$

The condition for sustained oscillation is

(20)

Obtained by equating the real part of eqn (2) to zero

$$\frac{L}{C_1} - \frac{(1+hfe)}{\omega^2 C_1 C_2} = 0 \rightarrow (8)$$

$$\frac{L}{C_1} = \frac{(1+hfe)}{\omega^2 C_1 C_2}$$

$$L = \frac{(1+hfe)}{\omega^2 C_2}$$

Substituting for ω^2 from eqn (4)

$$L = \frac{(1+hfe) L C_1 C_2}{C_2 (C_1 + C_2)}$$

$$L = \frac{(1+hfe) L C_1}{C_1 + C_2}$$

$$= C_1 C_2 = (1+hfe) C_1$$

$$C_1 \left[1 + \frac{C_2}{C_1} \right] = (1+hfe) C_1$$

$$hfe = \frac{C_2}{C_1} \rightarrow (9)$$

This is the condition for sustained oscillation.

(21)